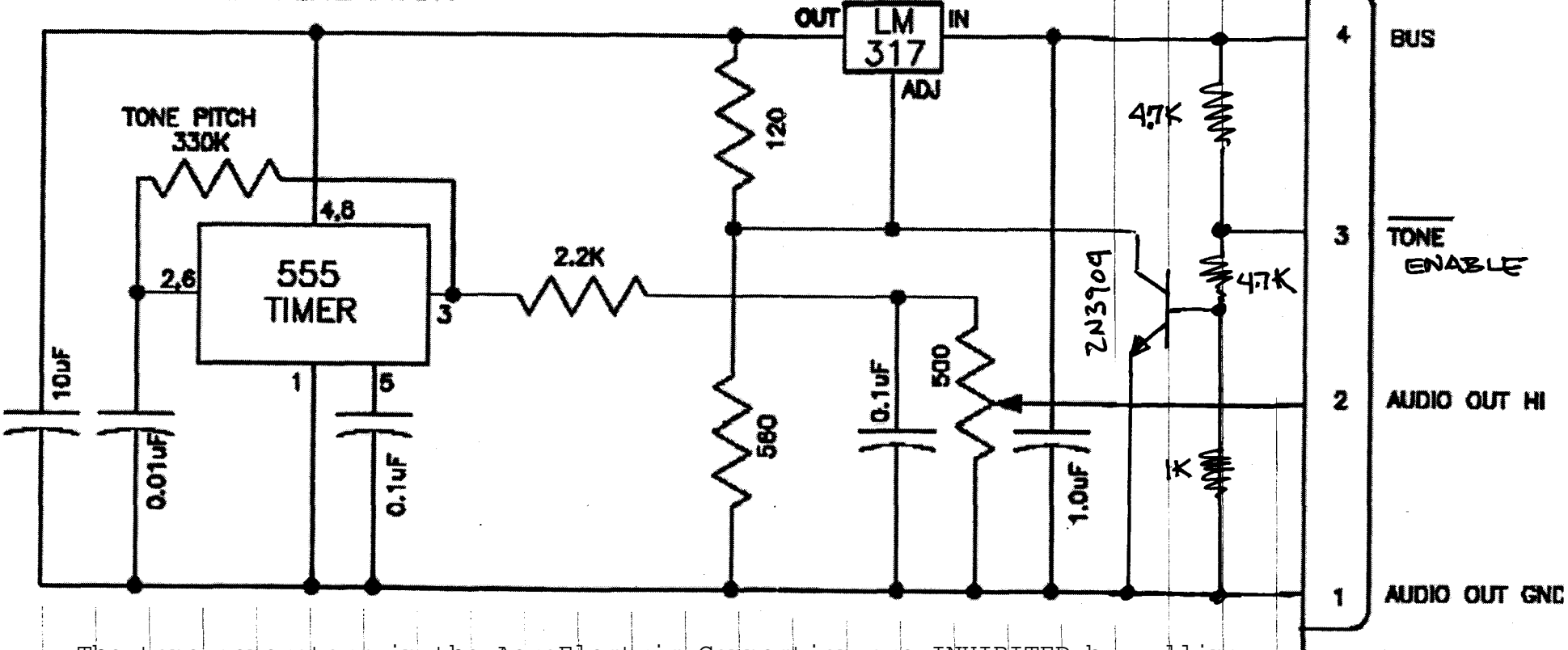


STEADY TONE GENERATOR



The tone generators in the AeroElectric Connection are INHIBITED by pulling the the control pin (3) to GROUND. There are some situations where it is handy to ENABLE generation of the tone by pulling pin 3 to ground. The schematic above proposes adding a small transistor, and three resistors (all available from Radio Shack) to invert the sense of the control signal. This same technique may be applied to any of the three styles of tone generator illustrated in Chapter 18 of The 'Connection.