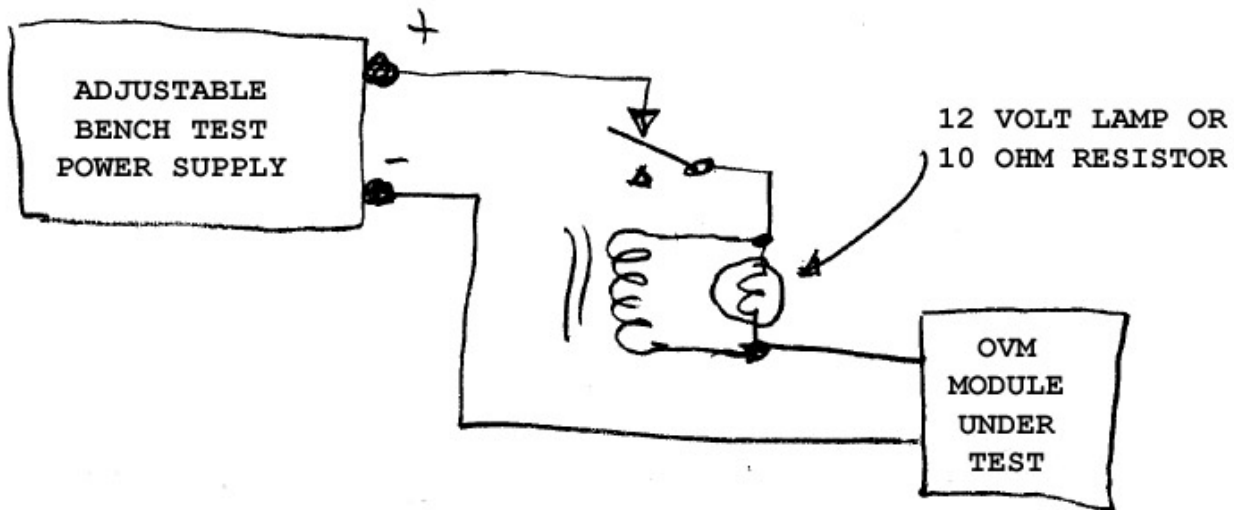


RELAY CAN BE ANY 12V POWER DEVICE LIKE THE S704-1, 30A PLASTIC SOLD BY B&C. MANY ELECTRONICS SUPPLIERS SELL SUITABLE DEVICES FOR \$3 OR SO. THE RELAY NEEDS TO HAVE SOME ADDITIONAL 'LOAD' IN THE FORM OF A 12 LAMP THAT DRAWS ABOUT 1 AMP, OR USE A 10 OHM, 5 WATT RESISTOR.

SET BENCH SUPPLY FOR 16.2 VOLTS AND ADJUST TRIGGER CALIBRATION POT ON CROWBAR OV MODULE SO THAT THE RELAY 'CLICKS' ABOUT ONCE PER SECOND.



CROWBAR OVM BENCH TEST FIXTURE